


159.233 Computer Architecture Assignment 1

Due date 27th March 2015

Design a basic Arithmetic/Logic Unit (ALU) that operates on two 2-bit binary numbers *a* and *b* and generates a third 2-bit number *s*.

The function of the ALU is determined by a 3-bit binary code *f*:

<i>f</i>	Name	Function
000	XOR	Logical Exclusive OR of <i>a</i> and <i>b</i>
001	AND	Logical AND of <i>a</i> and <i>b</i>
010	ADD	Add <i>a</i> to <i>b</i>
011	ADC	Add <i>a</i> to <i>b</i> and include <i>cin</i>
100	SUB	Subtract <i>b</i> from <i>a</i> (ignore <i>cin</i>)
101	SBC	Subtract (<i>b</i> + <i>cin</i>) from <i>a</i>
110	RSB	Subtract <i>a</i> from <i>b</i> (ignore <i>cin</i>)
111	RSC	Subtract (<i>a</i> + <i>cin</i>) from <i>b</i>

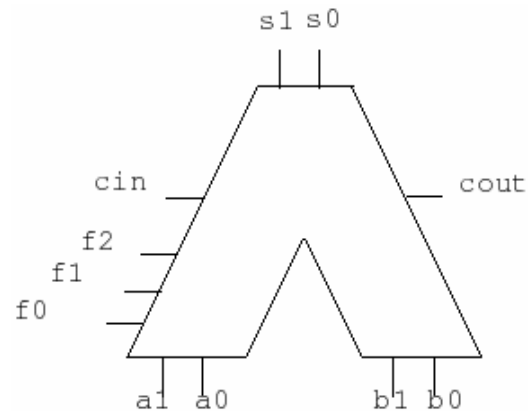

a0 is the least significant bit of *a*, *a1* is the most significant bit. For operations which do not use the carry input, it should be ignored. For operations which do not generate a carry (the first two), the carry output should be **zero**. If a carry occurs as a result of an addition, or a borrow occurs as a result of a subtraction, then *cout* should be 1.

Starting with the file **alu2015.lgf** (available on stream) add your design and test it using the switches labelled: *a0*, *a1*, *b0*, *b1*, *f0*, *f1*, *f2* and *cin* and the lights labelled *s0*, *s1* and *cout*. **Do NOT change or add anything inside the box in alu2015.lgf or use the “test” connection; if you do, you WILL lose marks.** You may only use basic gates (AND,OR,NOT,XOR,NOR,NAND) with any number of inputs. You **must** use the connections from the alu2014.lgf file. To do this, use the 'to' or 'from' devices in the catalogue. These allow you to make connections without drawing wires, simply click to assign a name to a connection and it will be connected to all other 'to' or 'from' devices with the same name. Your connections **must** be called *a0*, *a1*, *b0*, *b1*, *cin*, *f0*, *f1*, *f2*, *cout*, *s0* and *s1* so that they will connect to the test circuit. Do not add any switches to your design, you must be able to test your design by changing the switches on the left inside the box. Make sure the blue bars at the bottom of the log screen are not red before you submit your assignment.

This assignment is worth 10% of the final marks

Your assignment will be judged on accuracy and neatness.

Submit your alu.lgf file electronically from stream.

Make sure your name and id are displayed in your design.